

Electronic Devices & Circuits

Mid2 - Important questions – 1st DS A & B Sections

Syllabus : 3rd, 4th & 5th units

Subjective: After reading complete syllabus revise the following topics

1. Collector to base bias
2. Voltage divider bias
3. Generalized h-parameter model for BJT amplifier
4. Approximate h-parameter model for CE amplifier with emitter bypass capacitor.
5. Approximate h-parameter model for CE amplifier without emitter bypass capacitor.
6. JFET – Drain & Transfer characteristics
7. Enhancement MOSFET – Drain & Transfer characteristics
8. SCR – V-I Characteristics
9. Solar cell - V-I Characteristics
10. TUNNEL diode – V-I Characteristics
11. Numericals (Similar to that solved in class)

Objective: Direct questions will be given based on theory